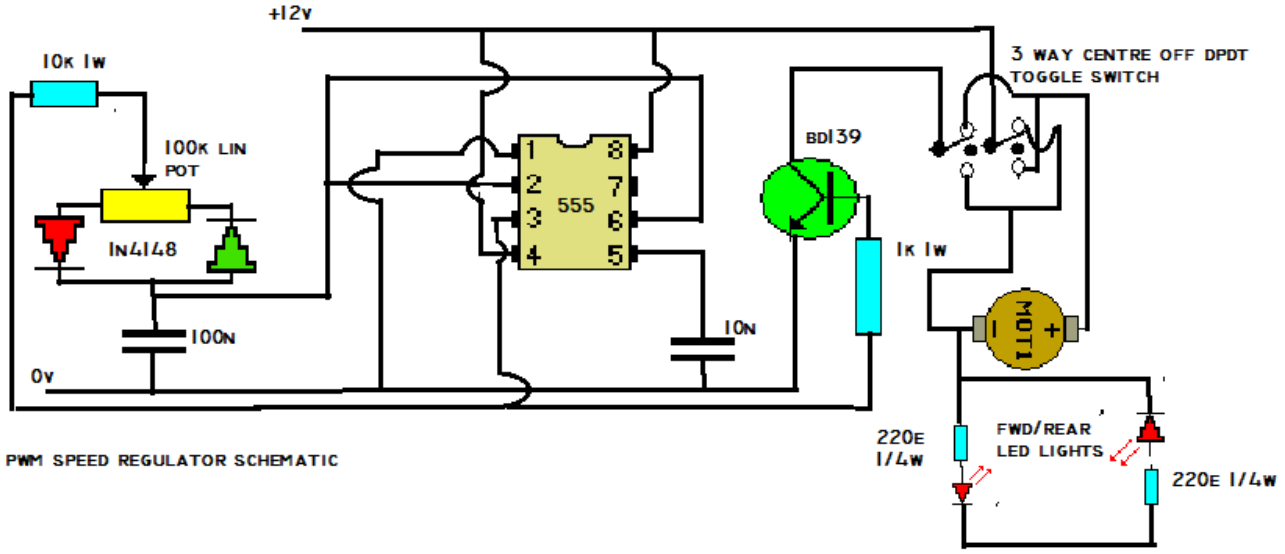

Manual PWM speed regulator

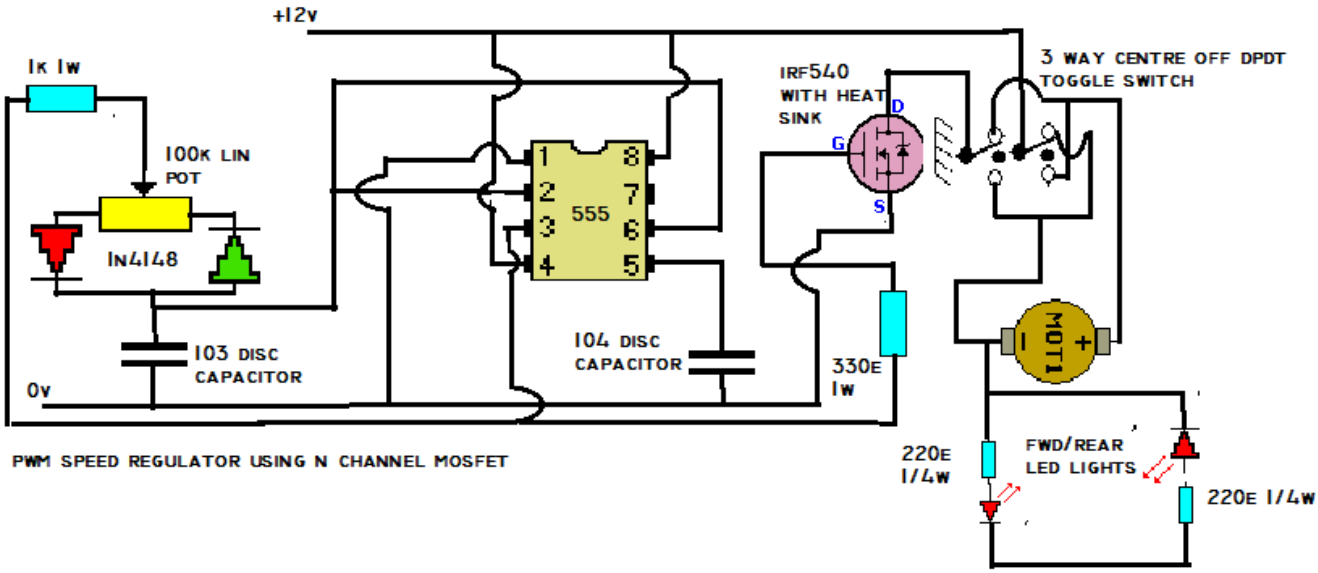

Manual PWM speed regulator using a MOSFET

Above are some suggested Manual PWM speed regulator schematics.

Disclaimer
Building these circuits require come knowledge of electronics and efficiency in working with electronic components, soldering techniques and other related small hand tools. We do not accept any responsibility for damage resulting from building or operation any of the circuits on this website. In no event Model Engineering Company or any of its associates will be liable to you for damages. Make sure you are comfortable at building electronic circuits, before you attempt in building the circuits on this website. Try at your own risk We are not responsible for any damage.